

```

1  `timescale 1ns / 1ns // `timescale time_unit/time_precision
2
3  // Morse code encoder with LED flash output
4  module MorseEncoder(input[9:0] SW, input[3:0] KEY, input CLOCK_50, output[9:0] LEDR);
5      wire[2:0] letterSelect;
6      wire PLoad,reset;
7
8      wire[12:0] MorseCode;
9      wire enableClock;
10     wire[24:0] rDivider;
11     wire flash;
12
13     // Input assignment
14     assign letterSelect = SW[2:0];
15     assign PLoad = KEY[1];
16     assign reset = KEY[0];
17
18     // Letter to Morse Code LUT
19     MorseTable MT0(.letterSelect(letterSelect),.MorseCode(MorseCode));
20
21     // Clock ever 0.5 seconds
22     rateDivider rD0(.clock(CLOCK_50),.reset(reset),.counter(rDivider));
23     assign enableClock = (rDivider==0);
24
25     // Shift register to display the morse code
26     shiftRegister reg0(.clock(CLOCK_50),.reset(reset),.PL(PLoad),
27                        .enable(enableClock),.DATA_IN(MorseCode),.leftBit(flash));
28
29     // Output
30     assign LEDR[0] = flash;
31 endmodule
32
33 // Left 13-bit shift register, inserts a 0 onto the right
34 // Active high async reset, active high async parallel load
35 module shiftRegister(input [12:0] DATA_IN, input reset,clock,PL,enable, output reg
leftBit);
36     reg[12:0] Q;
37
38     always @(posedge clock)
39     begin
40         if(reset) // Async reset
41         begin
42             Q <= 0;
43             leftBit <= 0;
44         end
45         else if(PL) // Async parallel load
46             Q <= DATA_IN;
47         else if(enable) // 0.5s clock pulse
48         begin // Do the shifting
49             leftBit <= Q[12];
50             Q[12] <= Q[11];
51             Q[11] <= Q[10];
52             Q[10] <= Q[9];
53             Q[9] <= Q[8];
54             Q[8] <= Q[7];
55             Q[7] <= Q[6];
56             Q[6] <= Q[5];
57             Q[5] <= Q[4];
58             Q[4] <= Q[3];
59             Q[3] <= Q[2];
60             Q[2] <= Q[1];
61             Q[1] <= Q[0];
62             Q[0] <= 0;
63         end
64     end
65 endmodule
66
67
68

```

```

69 // LUT for the Morse code of the selected letter (S-Z)
70 module MorseTable(input[2:0] letterSelect, output reg[12:0] MorseCode);
71     always @(*)
72     begin
73         case(letterSelect)
74             0: // S
75                 MorseCode = 13'b1010100000000;
76             1: // T
77                 MorseCode = 13'b1110000000000;
78             2: // U
79                 MorseCode = 13'b1010111000000;
80             3: // V
81                 MorseCode = 13'b1010101110000;
82             4: // W
83                 MorseCode = 13'b1011101110000;
84             5: // X
85                 MorseCode = 13'b1110101011100;
86             6: // Y
87                 MorseCode = 13'b1110101110111;
88             7: // Z
89                 MorseCode = 13'b1110111010100;
90             default: // Latch prevention
91                 MorseCode = 0;
92         endcase
93     end
94 endmodule
95
96 // Active high, synchronous reset positive edge triggered counter with parallel load
97 // Counts down from 25M-1 to 0, 25M is 25 bits
98 module rateDivider(input clock,reset, output reg[24:0] counter);
99     // When simulating use divisor = 1000000
100    // Uploading to FPGA use divisor = 1
101    // Used because simulating a 50 Mhz clock means a very long run time
102    parameter divisor = 1;
103
104    always @(posedge clock)
105    begin
106        if(reset) // Active high reset to loadIn
107            counter <= 2500000/divisor-1;
108        else if(counter==0) // Reset to initial value (1 cycle)
109            counter <= 2500000/divisor-1;
110        else // Count down
111            counter <= counter-1;
112    end
113 endmodule
114

```